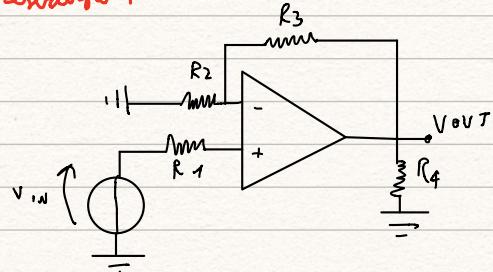


esercizio 1



$$Grade = \frac{G_{1d}}{1 - \frac{1}{G_{loop}}}$$

$$\begin{aligned}R_2 &= 10\text{ k}\Omega \\R_3 &= 10^6\text{ k}\Omega \\R_4 &= 10^6\text{ k}\Omega \\A_{diff} &\approx 120\text{ dB} (\approx 10^4)\end{aligned}$$

Opamp ideale $A_{diff} \rightarrow \infty$

RETROAZIONE NEGATIVA

1) Trasformatori reale $\frac{V_{out}}{V_{in}}$

$$\begin{aligned}-G_{1d} \\-G_{loop}\end{aligned} \quad (\text{H.P.: Opamp non ideale})$$

Calcolo G_{1d} :

$$i_{R_1} = 0 \rightarrow V^+ = V_{in}$$

$$V^- = V^+$$

$$V_{R_2} = V^- = V_{in}$$

$$i_{R_2} = \frac{V_{R_2}}{R_2} = \frac{V_{in}}{R_2}$$

$$i_{R_3} = i_{R_2} \rightarrow V_{R_3} = i_{R_3} \cdot R_3 = \frac{V_{in}}{R_2} \cdot R_3$$

$$V_{out} = V^- + V_{R_3} = V_{in} \left(1 + \frac{R_3}{R_2} \right)$$

$$G_{1d} = \left(1 + \frac{R_3}{R_2} \right) = 11$$


esempio

$$V_{in} = 100\text{ mV}$$

$$V_{out} = 1,1\text{ V}$$

$$V_{out} = V_{diff} A_{diff}$$

-G_{loop}

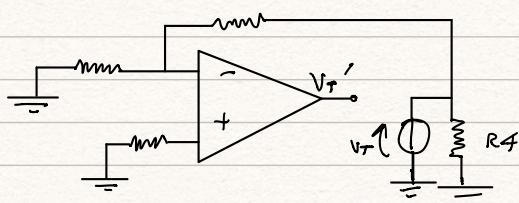

$$G_{loop} = \frac{V_T'}{V_T}$$

$$V^- = V_T \cdot \frac{R_2}{R_2 + R_3}$$

$$V^+ = 0$$

$$V_T' = (V^+ - V^-) \cdot A_{diff} = -A_{diff} \frac{R_2}{R_2 + R_3} \cdot V_T$$


$$G_{loop} = -A_{diff} \frac{R_2}{R_2 + R_3} = -90909$$

$$G_{loop} = \frac{G_{ID}}{1 - \frac{1}{G_{loop}}} = \frac{11}{1 - \frac{1}{(-90909)}} = 10,9998$$

3) Amplificatore rail to rail

$$V_{DD} = +15V \quad V_{SS} = -15V$$


Quanto vale la max corrente di uscita?

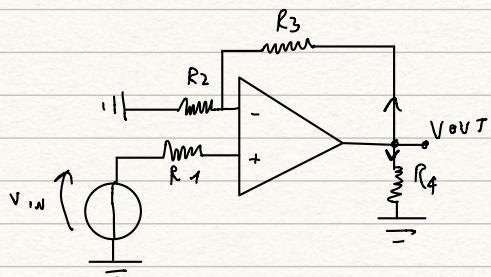

CASO PESSIMO PER $V_{OUT} = +15V$

$$I_{OUT} = I_{R_F} + I_{retroag} = V_{OUT} \left(\frac{1}{R_F} + \frac{1}{R_3 + R_2} \right) = 286,4 \mu A$$

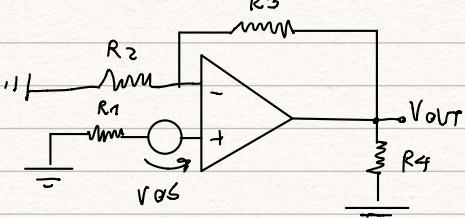
3) Voltaggio effetto su V_OUT di $V_{OS} = \pm 3,5 mV$



$$V^+ = V_{oss}$$

$$V^- = V^+$$
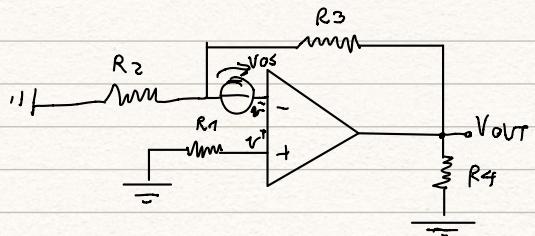
$$V_{out} = \pm V_{oss} \left(1 + \frac{R_3}{R_2} \right)$$



$$V^+ = 0$$

$$V^- = V^+$$

$$V_{R2} = -V_{oss} \rightarrow i_{R2} = -\frac{V_{oss}}{R_2}$$

$$V_{R3} = -\frac{V_{oss}}{R_2} R_3$$

$$V_{out} = \pm \left(V_{oss} \left(1 + \frac{R_3}{R_2} \right) \right) \approx \pm 27,5 \text{ mV}$$

4) Volutore effetto delle correnti di bias incanti e dell'offset di corrente dell'op.amp. sull'uscita


$$I_{BIAS} = \frac{I^+ + I^-}{2}$$

$$I_{os} = |I^+ - I^-|$$


$$I^+ = I_{BIAS} + \frac{I_{os}}{2}$$

$$I^- = I_{BIAS} - \frac{I_{os}}{2}$$


$$-I_{BIAS}$$

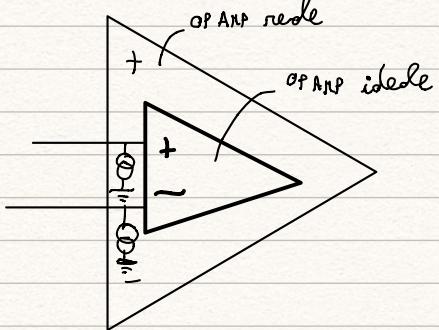

$$I_B^+ = I_B^- = I_{BIAS}$$

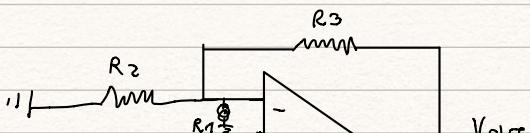

$$|V_{out}|_{I_B^+} = I_B^+ R_1 \left(1 + \frac{R_3}{R_2} \right)$$

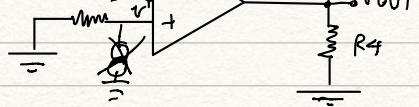


$$V_{\text{OUT}} | I_B = -I_B R_3$$

$$V_{\text{OUT}} = I_{\text{BIAS}} \left(R_1 \left(1 + \frac{R_3}{R_2} \right) - R_3 \right)$$

$$\text{Se } R_1 \left(1 + \frac{R_3}{R_2} \right) = R_3$$

$$V_{\text{OUT}} | I_{\text{BIAS}} = 0$$

- I_{OS}

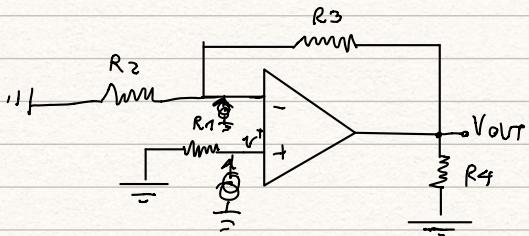


$$V_{\text{OUT}} | I_{\text{OS}}^+ = +I_{\text{OS}}^+ R_1 \left(1 + \frac{R_3}{R_2} \right)$$

$$V_{\text{OUT}} | I_{\text{OS}}^- = +I_{\text{OS}}^- R_3$$

$$|I_{\text{OS}}^+| = |I_{\text{OS}}^-| = \frac{|I_{\text{OS}}|}{2}$$

$$V_{\text{OUT}} | I_{\text{OS}} = \pm \frac{|I_{\text{OS}}|}{2} \left(R_1 \left(1 + \frac{R_3}{R_2} \right) + R_3 \right)$$

Exercise 2:

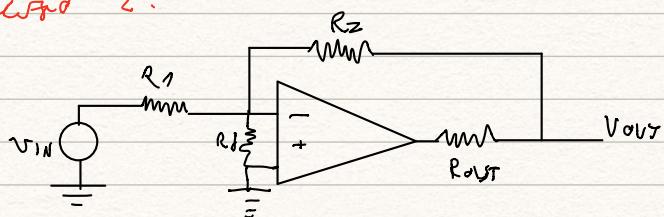

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 100 \text{ k}\Omega$$

$$R_f = 1 \text{ M}\Omega$$


$$R_{\text{OUT}} = 1 \text{ k}\Omega$$

$$A_{\text{diff}} = 100 \text{ dB} (10^5)$$

RETROAZIONE NEGATIVA

$$1) \text{ Girore} = \frac{V_{\text{OUT}}}{V_{\text{IN}}} | \text{ girore}$$

Giro:

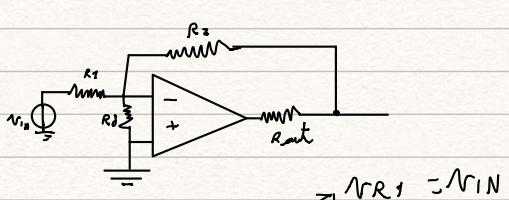

$$-V_{\text{R1}} = V_{\text{IN}}$$


$$I_{R_1} = \frac{V_{\text{IN}}}{R_1} = i R_2$$

$$V_{\text{OUT}} = \rho + (-V_{R_2}) = -V_{\text{IN}} \frac{R_2}{R_1}$$

$$v^- = v^+ = 0 \rightarrow i_{RD} = 0$$

$$\left| \frac{V_{OUT}}{V_{IN}} \right|_{ID} = -\frac{R_2}{R_1}$$

- Gloop

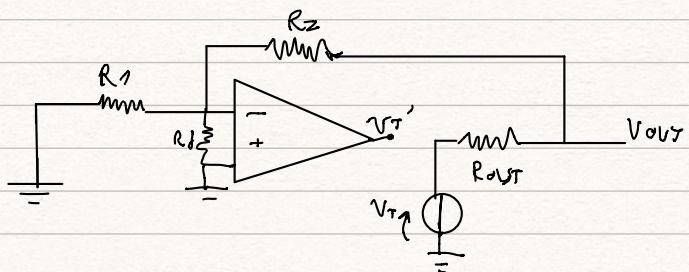

$$\frac{v_T'}{v_T} = G_{loop}$$


$$v^- = v_T - \frac{R_1 // R_d}{(R_1 // R_d) + R_2 + R_{OUT}}$$

$$v_T' = -v^- A_{diff}$$


$$G_{loop} = -A_{diff} \frac{R_1 // R_d}{(R_1 // R_d) + R_2 + R_{OUT}} = -8927$$

$$G_{rade} = \frac{G_{loop}}{1 - \frac{1}{slope}} = 9,9$$

2) Voltovee zin e zout

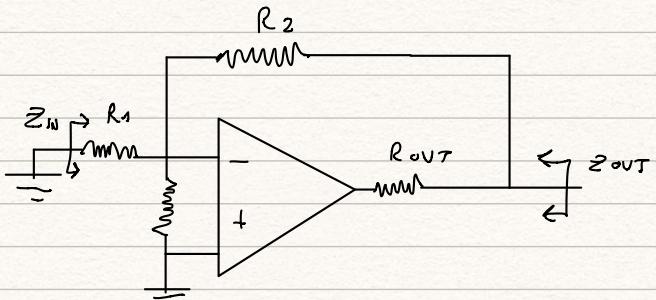

z_{in}

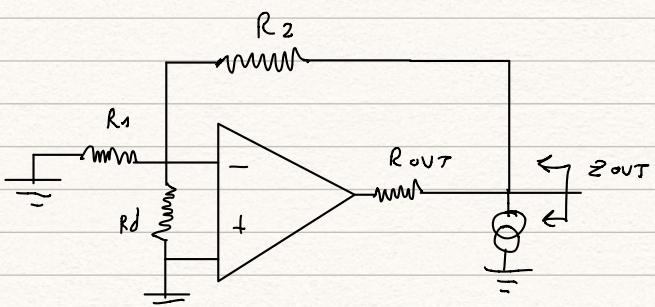


$$Z_{out} = \frac{Z_{out}}{1 - G_{loop}}$$

$$Z_{out}^0 = R_{out} \parallel \left[R_2 + \left(R_1 / (R_d) \right) \right] = 991 \Omega$$

$$Z_{out} = \frac{991 \Omega}{1 + 8927} = 9.11 \Omega$$

Z_{in}

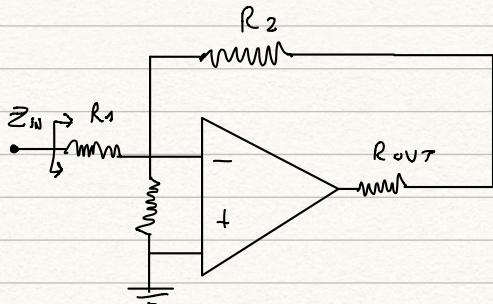


$$Z_{in} = R_1 + R_d \parallel Z^*$$

$$Z^* = \frac{Z^0}{1 - G_{loop}^*}$$


$$Z^0 = R_2 + R_{out}$$

$$G_{loop}^* = -A_{diff}$$
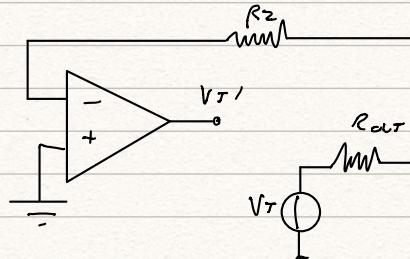
$$Z^* = \frac{R_2 + R_{out}}{1 + A_{diff}} = 1.01 \Omega$$


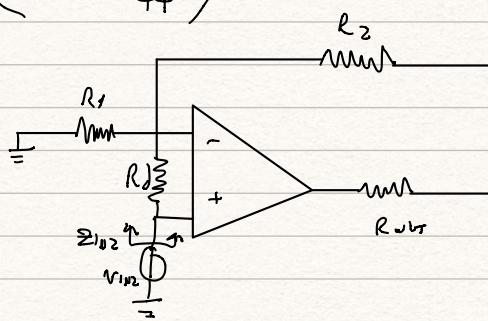
$$Z_{in} = R_1 + R_d \parallel \left(\frac{R_2 + R_{out}}{1 + A_{diff}} \right)$$



retroazione $i_{R_d} \rightarrow 0$


$$Z_{in1} = Z_{in2}^0 (1 - G_{loop})$$

$$Z_{IN\ 2^{\circ}} = R_d + \left[R_1 \parallel \left(R_2 + R_{OUT} \right) \right]$$

$$G_{loop} = -\frac{R_1 \parallel R_d}{R_1 \parallel R_d + R_2 + R_{OUT}} \quad A_{diff} \approx -8927$$

$$Z_{IN\ 2} \approx 1\text{M}\Omega \left(1 + 8927 \right) = 8928\text{M}\Omega$$

esercizio 3:

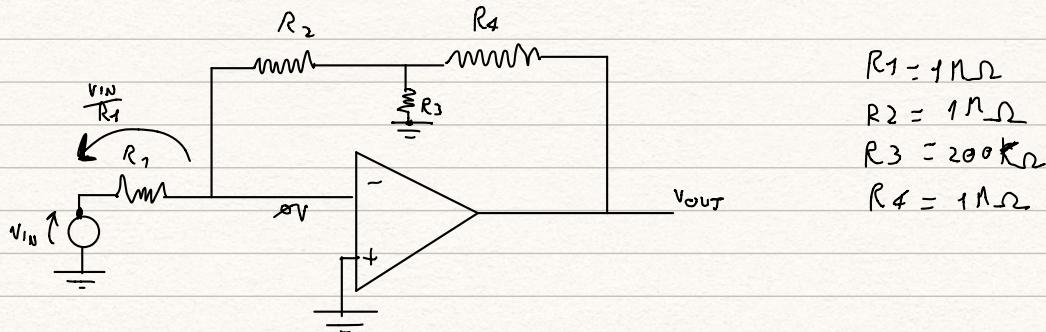

7) G_{ID}

$$iR_1 = iR_2$$

$$V_{R3} = -V_{IN} \frac{R_2}{R_1}$$

$$i_{R3} = -V_{IN} \frac{R_2}{R_1}$$

$$\frac{R_3}{R_3}$$


$$i_{R4} = i_{R2} - i_{R3} = \frac{V_{IN}}{R_1} - \left(-\frac{V_{IN}}{R_3} \frac{R_2}{R_1} \right) =$$

$$= V_{IN} \left(\frac{1}{R_1} + \frac{R_2}{R_3 R_1} \right)$$

$$V_{R4} = \frac{V_{IN}}{R_1} \left(1 + \frac{R_2}{R_3} \right) R_4$$

$$V_{OUT} = -V_{IN} \frac{R_2}{R_1} - \frac{V_{IN} R_4}{R_1} \left(1 + \frac{R_2}{R_3} \right) = V_{IN} \left(-\frac{R_2}{R_1} + \frac{R_4}{R_1} + \frac{R_4}{R_1} \cdot \frac{R_2}{R_3} \right)$$

esercizio 4:

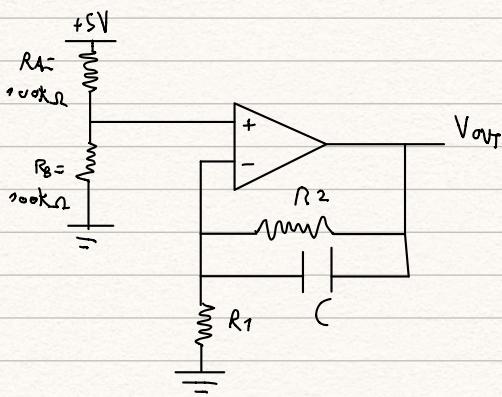


$$\begin{aligned}
 R_2 &= 2\text{k}\Omega \\
 R_1 &= 1\text{k}\Omega \\
 C &= 5\text{pF} \\
 A_{diff} &= 100\text{dB} (\rightarrow 10^5) \\
 CMRR &= 80\text{dB}
 \end{aligned}$$

$$\left(\frac{A_{diff}}{A_{CM}} = CMRR \rightarrow \frac{10^5}{A_{CM}} = 10^5 \rightarrow A_{CM} = 10 \right)$$

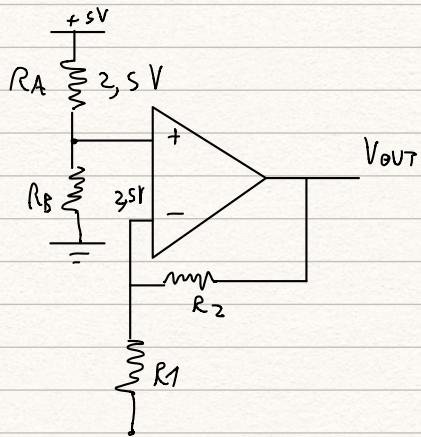7) Con $i_{IN} = 0$

Voltmetro effettua su V_{OUT} solo modo comm. di ingresso



$$V_{OUT} = 2.5 \text{ V} \left(1 + \frac{R_2}{R_A}\right) = 7.5 \text{ V}$$

$$V_{CN} = 2.5 \text{ V}$$